

Pin Number On Arduino	Connected To
A0	Not Connected
A1	Trig Pin
A2	Echo Pin
A3	Not Connected
A4	Not Connected
A5	Not Connected
0	Not Connected
1	Not Connected
2	Trig Pin
3	Not Connected
4	Echo Pin
5	IN2
6	IN1
7	IN2
8	IN3
9	IN4
10	IN1
11	A+
12	IN3
13	IN4
GND	A-

Chip
Not Connected
Back Ultrasonic Sensor
Back Ultrasonic Sensor
Not Connected
Not Connected
Not Connected
Not Connected
Not Connected
Front Ultrasonic Sensor
Not Connected
Front Ultrasonic Sensor
H-Bridge (CKT2) (L298N)
H-Bridge (CKT1) (L298N)
H-Bridge (CKT1) (L298N)
H-Bridge (CKT1) (L298N)
H-Bridge (CKT1) (L298N)
H-Bridge (CKT2) (L298N)
Class D amplifier - Speaker For Active Feedback
H-Bridge (CKT2) (L298N)
H-Bridge (CKT2) (L298N)
Class D amplifier - Speaker